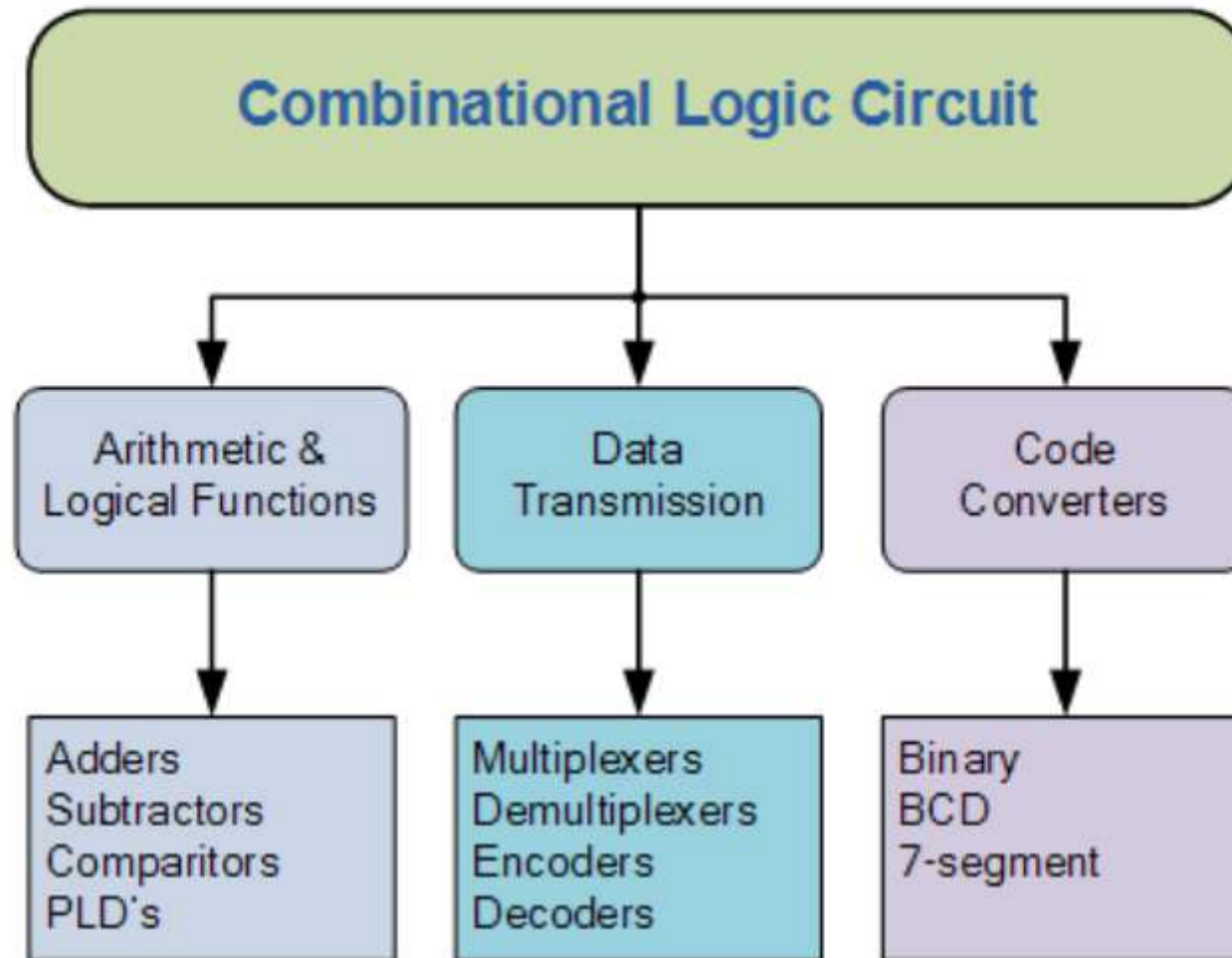


Outline

- ◆ Design Combinational Logic Circuit for scenario
- ◆ Adder
- ◆ Subtractor
- ◆ Comparator
- ◆ Multiplexer
- ◆ Demultiplexer
- ◆ Encoder
- ◆ Decoder
- ◆ Code Conversions
- ◆ Implementation



Application of CLC




Introduction

LOGIC CIRCUITS: $\left\{ \begin{array}{l} 1. \text{ Combinational} \\ 2. \text{ Sequential} \end{array} \right.$

Combinational Logic Circuits (Circuits without a memory): In this type of logic circuits outputs depend only on the current inputs.

Sequential Logic Circuits (Circuits with memory): In this type of logic circuits outputs depend on the current inputs and previous inputs. These circuits employ storage elements and logic gates.

Combinational Logic Circuits

 

- ◆ A combinational circuit consists of **input variables (n)**, **logic gates**, and **output variables (m)**.
- ◆ For (n) input variables there are 2^n possible combinations of binary input values.
- ◆ For each possible input combination there is one and only one possible output combination, a combinational circuit can be describe by (m) Boolean functions one for each output variable.
- ◆ Each output function expressed in terms of the (n) input variables.

Adders

- ◆ Digital computers perform a variety of information processing tasks. Among the basic functions encountered are the various *arithmetic operations (addition)*.


Binary Arithmetic

1. Addition: The rules of addition are:


$0 + 0 = 0$
$0 + 1 = 1$
$1 + 0 = 1$
$1 + 1 = 10$
$1 + 1 + 1 = 11$



The block diagram for the half adder is:

 

(a) $S = xy' + x'y$
 $C = xy$

 

(b) $S = x \oplus y$
 $C = xy$

Binary Adder -Full Adder

Q/Design a combinational logic circuit that performs arithmetic operation for adding three bits?


Answer: $n=3\text{bit}$, $n=2^3=8$

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




X \ YZ	00	01	11	10
0		1		1
1	1		1	
 
$$S = \overline{X}YZ + \overline{X}Y\overline{Z} + X\overline{Y}Z + XYZ$$



X \ YZ	00	01	11	10
0			1	
1		1	1	1

$$C = XY + XZ + YZ$$

 

The block diagram for the full adder is:



Subtractor

- ◆ Digital computers perform a variety of information processing tasks. Among the basic functions encountered are the various *arithmetic operations (Subtraction)*.

Binary Arithmetic

2. Subtraction: The rules of subtractions are:

$$0 - 0 = 0$$

$$1 - 0 = 1$$

$$10 - 1 = 1$$

$$1 - 1 = 0$$



Binary Subtractor- Half Subtractor

Q/Design a combinational logic circuit that performs arithmetic operation for subtracting two bits?

Answer: $n = 2\text{bit}$, $n = 2^2 = 4$

$$0 - 0 = 0$$

$$1 - 0 = 1$$




$$1 - 1 = 0$$

$$0 - 1 = 10 - 1 = 1 \quad (\text{The 1 borrowed from the next higher stage})$$

Inputs		Outputs	
X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$D = \bar{X}Y + X\bar{Y} = X \oplus Y$$

$$B = \bar{X}Y$$

   

Binary Subtractor – Full Subtractor

Q/Design a combinational logic circuit that performs arithmetic operation for subtracting three bits?

Answer: $n=3\text{bits}$, $n=2^3=8$

Inputs			Outputs	
X	Y	Z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1





		yz		y	
		00	01	11	10
x	0		1		1
x	1	1		1	

$$D = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$


		yz		y	
		00	01	11	10
x	0		1	1	1
x	1			1	

$$B = \bar{X}Y + \bar{X}Z + YZ$$

  

Multiplexer (Data Selector)

 Multiplexing means transmitting a large number of information units over a smaller number of channels or lines. A digital multiplexer is CLC that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by of a selection lines.



Design MUX:

AND gates used to represent inputs.

One **OR** gate only used to collect inputs.


NOT gates as a selector to connect inputs to output.

Example: Design 4 x 1 multiplexer?


Solution: No. of inputs = $4 = 2^2$, No. of select=2, No. of output=1

Select		Output
s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Truth Table

 

Block diagram

 

4x1 Multiplexer Logic Diagram