

① Kirchoff's Laws:-

1st Law:- The sum of voltage drops around a closed loop is equal to sum of voltage sources of that loop. [Voltage law]



• Closed loop must have 2 conditions:-

- (i) It must have one or more voltage sources.
- (ii) It must have a complete path for current flow from any point, around loop, & back to that point.



② 2nd Law:- The current arriving at any junction point in circuit is equal to current leaving that junction (Kirchoff's current law).

* Sign Convention:-

(a) For emf:-

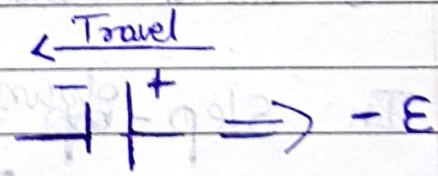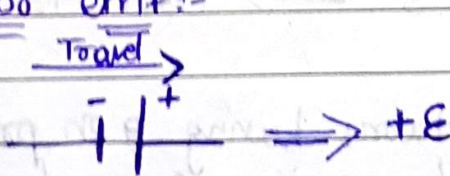

(b) For resistor:-

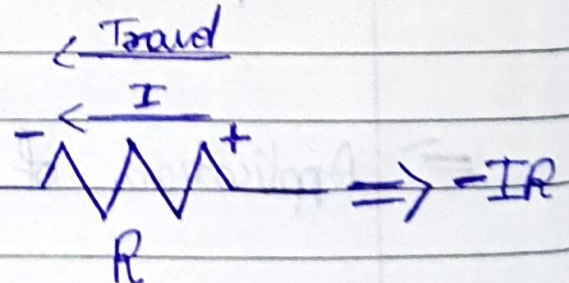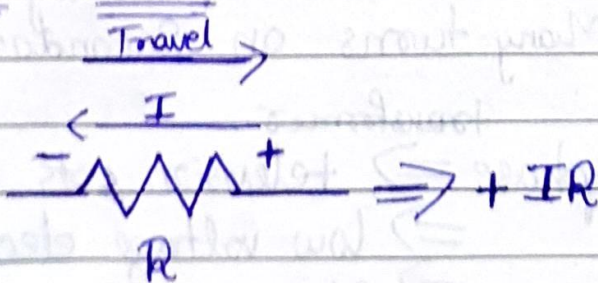

* Faraday's Laws of Electromagnetic Induction.

• Consists of 2 laws:-

• 1st Law:- Whenever a conductor is placed in a varying M.F., an emf is induced.

If conductor circuit is closed, a current is induced which is called induced current.

• 2nd Law:- The induced emf in a coil is equal to the rate of change of flux linkage.

* Transformer:- is working on principle of electromagnetic induction i.e. when current in 1 circuit changes, an induced current is set up in neighbouring circuit.

• Consists of 2 coils \Rightarrow primary & secondary.

• To avoid eddy currents \Rightarrow core is laminated.

• In Step-~~down~~^{up} \Rightarrow Many turns having ϕ on primary coil
 \Rightarrow few turns on secondary coil.

• Step-~~down~~^{up} \Rightarrow few turns on primary coil.
 \Rightarrow Many turns on secondary coil.

\Rightarrow Applications of Single-phase ^{transformer} \Rightarrow television sets to regulate voltage
 \Rightarrow low voltage electronic devices
 \Rightarrow Step-up power in home inverter.

- $I = \frac{V}{Z}$

- $Z = \sqrt{R^2 + (X_L - X_C)^2}$

- DC circuit \Rightarrow product of voltage & current \Rightarrow power.

- AC circuit \Rightarrow product of RMS value of voltage & current gives Volt-Ampere & true power. \Rightarrow apparent power.

- Apparent power \Rightarrow 2 components \Rightarrow ① True power / Active power
② Reactive power.

* In single phase a.c. system:-

- | | | |
|------------------|---|---------|
| ① True power | $P = VI \cos \phi$ | (watts) |
| ② Reactive power | $P = VI \sin \phi$ | (VAR) |
| ③ Apparent power | $P_a = V \cdot I$
$= (V \cdot I \cos \phi) + j(V \cdot I \sin \phi)$ | |

* In three phase a.c. system:-

- | | | |
|--------------|----------------------------------|---------|
| ① True power | $P = \sqrt{3} V_L I_L \cos \phi$ | (watts) |
| | $= \sqrt{3} V_p I_p \cos \phi$ | (watts) |

- Wattmeter \Rightarrow measure electrical power.

• Wattmeter consists of 2 coils :-

- ① Current coil (C.C) :- \rightarrow connected in series of load
 \rightarrow carries full load current.
 \rightarrow very low resistance
 \rightarrow few no. of turns of thick conductor
- ② Potential coil (P.C) :- \rightarrow connected in parallel of load
(Pressure coil) \rightarrow high resistance
 \rightarrow large no. of turns of thin conductor.

\Rightarrow 3-phase have 3 system:-

- ① 1 wattmeter method \rightarrow ^{Total} power is 3 time of that measured by ^{Single wattmeter}
- ② 2 wattmeter method \rightarrow TP is sum of 2 WM, both for ^{balanced} _{unbalanced}
- ③ 3 wattmeter method \rightarrow Algebraic sum of 3 WM will give Total power.

* Gates :-

IC 7408

① AND $\rightarrow Y = A \cdot B$ [Both ⁱⁿ input is ⁽¹⁾ high then output is ^{high}]

IC 7432

② OR $\rightarrow Y = A + B$ [Both input is ⁽⁰⁾ low then output is ^{low}]

IC 7404

③ NOT $\rightarrow Y = \bar{A}$ [produces complement of its input] [INVERTER]

IC 7400

④ NAND $\rightarrow Y = \overline{A \cdot B}$ [Both input is ⁽¹⁾ high then output is ⁽⁰⁾ low]

IC 7402

⑤ NOR $\rightarrow Y = \overline{A + B}$ [Both input is ⁽⁰⁾ low then out put is ⁽¹⁾ high]

\Rightarrow Universal Gate \Rightarrow NAND & NOR

\Rightarrow create any logical Boolean expression using only NOR or only NAND gates.

IC 7486


⑥ Exclusive OR (X-OR) $\rightarrow Y = A \oplus B \Rightarrow \bar{A}B + A\bar{B}$
 \Rightarrow [When no. of 1's at its inputs is odd, output is 1]
 \Rightarrow [Same input \Rightarrow output low]

IC 74286

⑦ Exclusive NOR (X-NOR) $\rightarrow Y = A \odot B \Rightarrow \bar{A}\bar{B} + AB$
 \Rightarrow [When no. 1's at its input is not odd,
 \Rightarrow [Same input \Rightarrow output high] Output is 1]

- Diodes \rightarrow 2 terminal devices having 2 diff types of semiconductors joined together forming only a single junction.

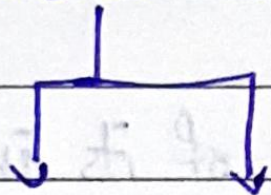- Transistor \rightarrow 3 terminal device $\left. \begin{array}{l} \text{Base} \\ \text{collector} \\ \text{emitter} \end{array} \right\}$



BJT

Bipolar junction Trans.

FET \rightarrow Field Effect Trans.

- ① SR-Flip Flop ② Delay Flip Flop ③ J-K Flip Flop ③ T Flip Flop