

Name : Hunaid Siamwala S.

Subject : Physics

Subject Code : 102001213

Class : 2-CE-1

Enrollment No : 12002040701067

13/5/21

1200200701067 (1)
Humaid

★

Experiment - 2 [Forward Bias]


Objective: Study of characteristics of Zener Diode in forward bias.

Equipments

needed: Measurement unit, patch cords

Procedure:

1. Before switch 'ON' measurement unit, connect the circuit as shown in Figure.
2. Switch 'ON' the power supply.
3. Rotate Potentiometer P_1 fully in counter clockwise direction.
4. Vary the potentiometer P_1 so as to increase the value of diode V_D from 0 to 1V in step 2 measure the corresponding values of diode current I_D in an Observation Table.
5. Plot a curve between diode voltage V_D & current I_D as shown in nature of graph.

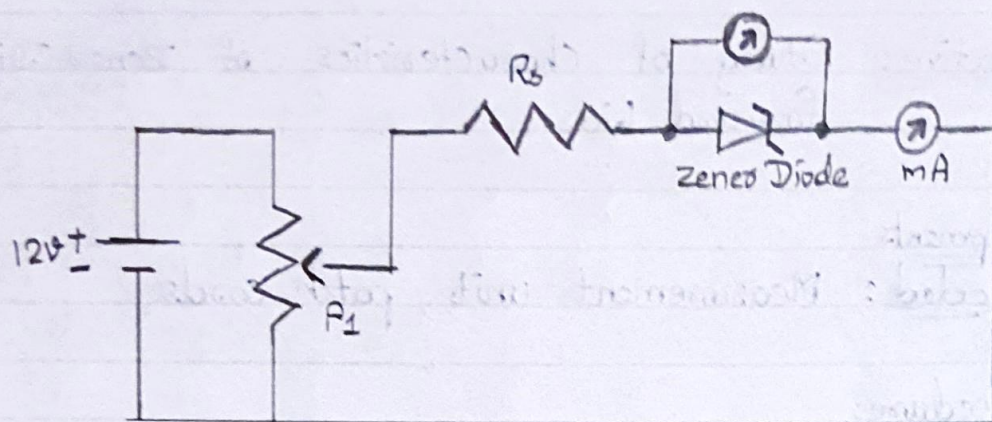Circuit Diagram:- Forward Bias (Zener)Observation Table:-

Sr. No	Diode Voltage V_D (Volts)	Diode Current I_D (mA)
1.	0.10	0.0
2.	0.21	0.0
3.	0.33	0.0
4.	0.41	0.0
5.	0.48	0.94 (knee Voltage)
6.	0.66	5.94
7.	0.77	11.21

* [Reverse Bias]

Objective:- Study of characteristics of Zener diode in reverse bias.

Equipments


needed:- Measurement unit, patch cords.

Procedure:-

1. Before switch 'ON' measurement unit, connect the circuit as shown in figure.
2. Switch 'ON' the power supply.
3. Rotate potentiometer P_1 fully in counter clockwise direction.
4. Vary the potentiometer P_2 so as to increase the value of diode V_D from 1V to 12V in step 2 measure the corresponding values of diode current I_D in an Observation Table.
5. Plot a curve between diode voltage V_D & current I_D as shown in nature of graph.

Conclusion:-


- We can conclude how zener diode works in forward & in Reverse bias. Also we can able to know about the breakdown voltage.

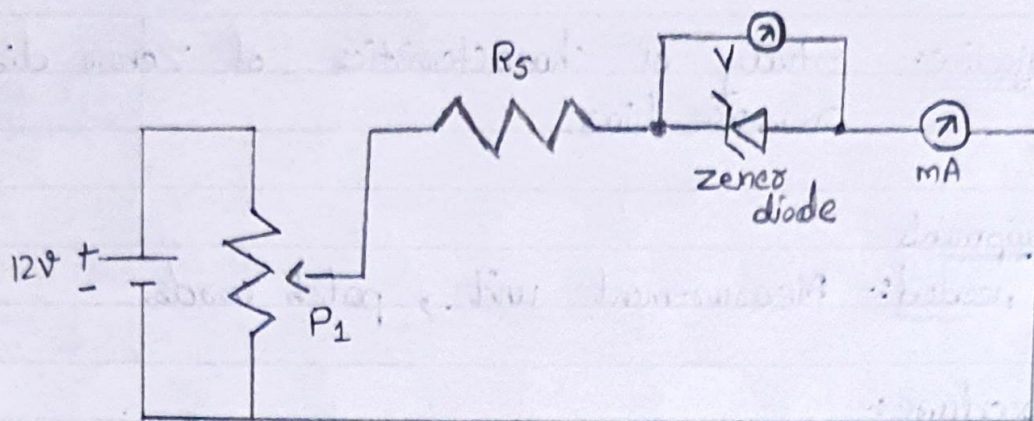Circuit Diagram :- Reverse Bias (Zener)Observation Table :-

So. No.	Diode Voltage V_D (Volts)	Diode Current I_D (mA)
1.	1.0	0.0
2.	2.1	0.0
3.	3.05	0.0
4.	4.0	0.0
5.	5.0	0.0
6.	6.1	0.0
7.	7.0	0.0
8.	8.0	0.0
9.	8.5	0.53
10.	9.0	07.6

(breaking current)

Zener Forward Bias

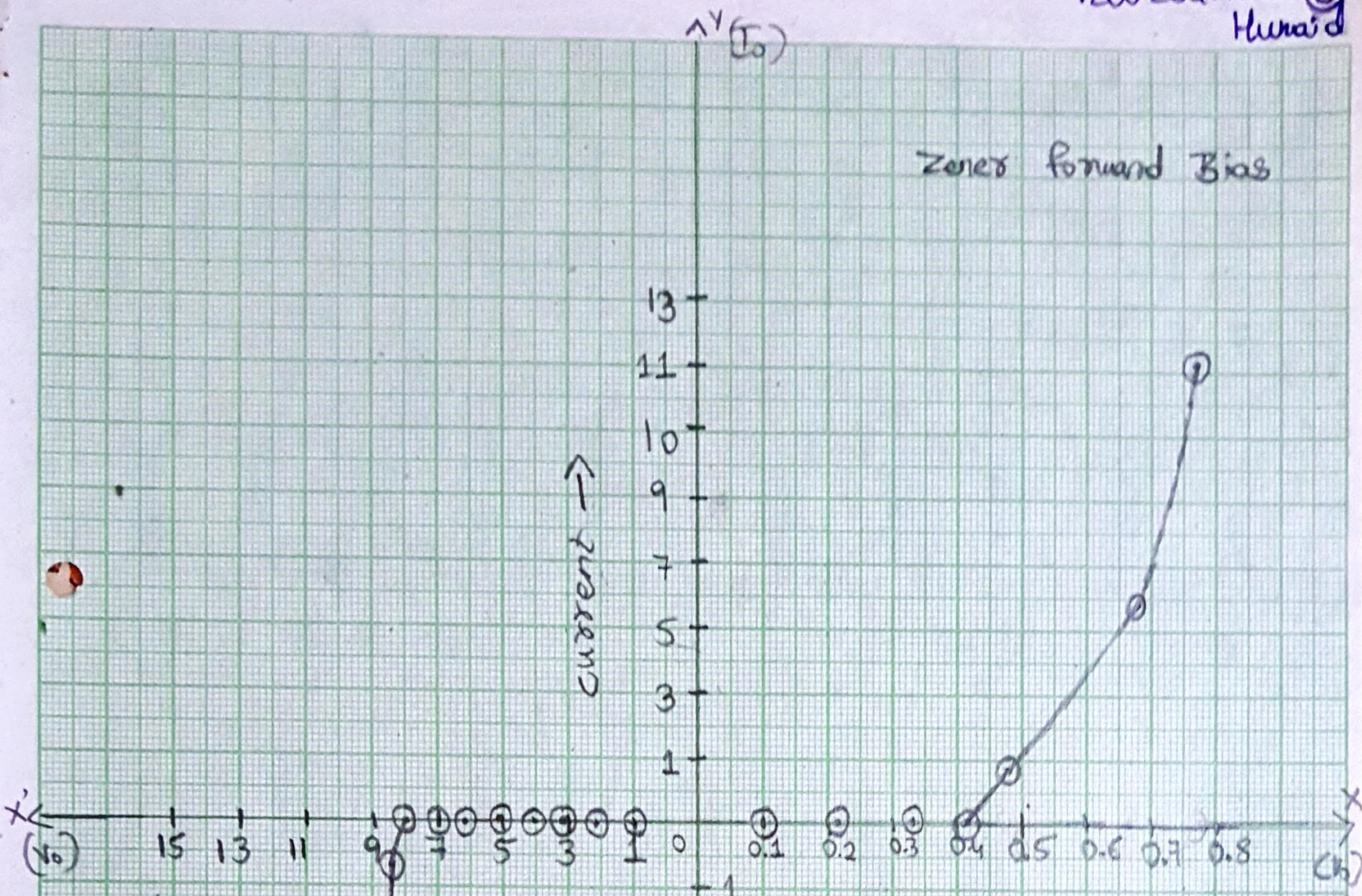

current \uparrow

Volts \rightarrow

Zener Reverse Bias

