

---

# Digital Logic Design

## Chapter 2

Boolean Algebra and Logic Gate

## 2.2 BASIC DEFINITIONS

- A set is collection of elements having the same property.
  - ◆  $S$ : set,  $x$  and  $y$ : element or event
  - ◆ For example:  $S = \{1, 2, 3, 4\}$ 
    - » If  $x = 2$ , then  $x \in S$ .
    - » If  $y = 5$ , then  $y \notin S$ .
- A binary operator defines on a set  $S$  of elements is a rule that assigns, to each pair of elements from  $S$ , a unique element from  $S$ .
  - ◆ For example: given a set  $S$ , consider  $a * b = c$  and  $*$  is a binary operator.
  - ◆ If  $(a, b)$  through  $*$  get  $c$  and  $a, b, c \in S$ , then  $*$  is a binary operator of  $S$ .
  - ◆ On the other hand, if  $*$  is not a binary operator of  $S$  and  $a, b \in S$ , then  $c \notin S$ .

# 2.1 Algebras

## ▣ What is an algebra?

- ◆ Mathematical system consisting of
  - » Set of elements (example:  $N = \{1, 2, 3, 4, \dots\}$ )
  - » Set of operators (+, -, ×, ÷)
  - » Axioms or postulates (associativity, distributivity, closure, identity elements, etc.)

## ▣ Why is it important?

- ◆ Defines rules of “calculations”

## ▣ Note: operators with two inputs are called binary

- ◆ Does not mean they are restricted to binary numbers!
- ◆ Operator(s) with one input are called unary

# BASIC DEFINITIONS

▣ The common postulates used to formulate algebraic structures are:

**1. Closure:** a set  $S$  is closed with respect to a binary operator if, for every pair of elements of  $S$ , the binary operator specifies a rule for obtaining a unique element of  $S$ .

◆ *For example, natural numbers  $N=\{1,2,3,\dots\}$  is closed w.r.t. the binary operator  $+$  by the rule of arithmetic addition, since, for any  $a, b \in N$ , there is a unique  $c \in N$  such that*

»  $a+b = c$

» But operator  $-$  is not closed for  $N$ , because  $2-3 = -1$  and  $2, 3 \in N$ , but  $(-1) \notin N$ .

**2. Associative law:** a binary operator  $*$  on a set  $S$  is said to be associative whenever

◆  $(x * y) * z = x * (y * z)$  for all  $x, y, z \in S$

»  $(x+y)+z = x+(y+z)$

**3. Commutative law:** a binary operator  $*$  on a set  $S$  is said to be commutative whenever

◆  $x * y = y * x$  for all  $x, y \in S$

»  $x+y = y+x$

# BASIC DEFINITIONS

**4. Identity element:** a set  $S$  is said to have an identity element with respect to a binary operation  $*$  on  $S$  if there exists an element  $e \in S$  with the property that

◆  $e * x = x * e = x$  for every  $x \in S$

»  $0 + x = x + 0 = x$  for every  $x \in I$   $I = \{..., -3, -2, -1, 0, 1, 2, 3, ...\}$ .

»  $1 \times x = x \times 1 = x$  for every  $x \in I$   $I = \{..., -3, -2, -1, 0, 1, 2, 3, ...\}$ .

**5. Inverse:** a set having the identity element  $e$  with respect to the binary operator to have an inverse whenever, for every  $x \in S$ , there exists an element  $y \in S$  such that

◆  $x * y = e$

» The operator  $+$  over  $I$ , with  $e = 0$ , the inverse of an element  $a$  is  $(-a)$ , since  $a + (-a) = 0$ .


**6. Distributive law:** if  $(*)$  and  $(.)$  are two binary operators on a set  $S$ ,  $(*)$  is said to be distributive over  $(.)$  whenever

◆  $x * (y.z) = (x * y).(x * z)$

# George Boole
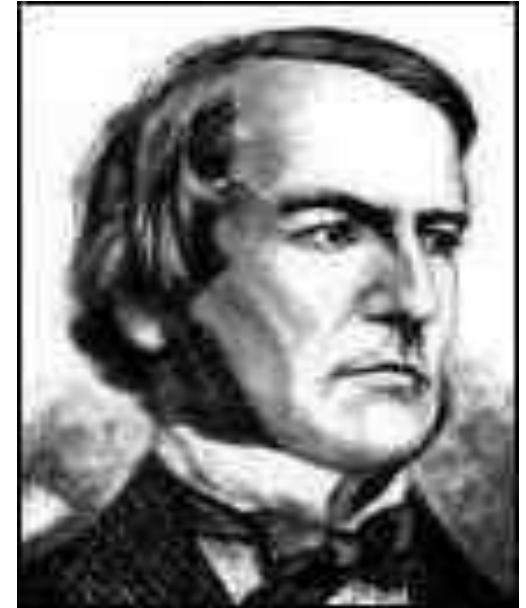
## ■ Father of Boolean algebra

- He came up with a type of linguistic algebra, the three most basic operations of which were (and still are) **AND, OR and NOT**. It was these three functions that formed the basis of his premise, and were the only operations necessary to perform comparisons or basic mathematical functions.
- Boole's system was based on a binary approach, **processing only two objects - the yes-no, true-false, on-off, zero-one approach.**
- Surprisingly, given his standing in the academic community, Boole's idea was either criticized or completely ignored by the majority of his peers.
- Eventually, one bright student, **claud shunnon**(1916-2001), picked up the idea and ran with it



George Boole (1815 - 1864)

## 2.3 Axiomatic Definition of Boolean Algebra

- We need to define algebra for binary values
  - ◆ Developed by George Boole in 1854
- Huntington postulates (1904) for Boolean algebra :
- $B = \{0, 1\}$  and two binary operations,  $(+)$  and  $(\cdot)$ 
  - ◆ Closure with respect to operator  $(+)$  and operator  $(\cdot)$
  - ◆ Identity element 0 for operator  $(+)$  and 1 for operator  $(\cdot)$
  - ◆ Commutativity with respect to  $(+)$  and  $(\cdot)$

$$x+y = y+x, \quad x \cdot y = y \cdot x$$

- ◆ Distributivity of  $(\cdot)$  over  $(+)$ , and  $(+)$  over  $(\cdot)$

$$x \cdot (y+z) = (x \cdot y) + (x \cdot z) \quad \text{and} \quad x + (y \cdot z) = (x+y) \cdot (x+z)$$

- Complement for every element  $x$  is  $x'$  with  $x+x'=1$ ,  $x \cdot x'=0$
- ◆ There are at least two elements  $x, y \in B$  such that  $x \neq y$

# Boolean Algebra

---

## □ Terminology:

- ◆ *Literal*: A variable or its complement
- ◆ *Product term*: literals connected by ( $\cdot$ )
- ◆ *Sum term*: literals connected by ( $+$ )



# Postulates of Two-Valued Boolean Algebra

- ▣  $B = \{0, 1\}$  and two binary operations,  $(+)$  and  $(\cdot)$
- ▣ The rules of operations: AND, OR and NOT.

## AND

$x$	$y$	$X \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

## OR

$x$	$y$	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

## NOT

$x$	$X'$
0	1
1	0

1. Closure ( $+$  and  $\cdot$ )
2. The identity elements
  - (1)  $x + 0 = x$
  - (2)  $x \cdot 1 = x$

# Postulates of Two-Valued Boolean Algebra

3. The commutative laws  $x+y = y+x$ ,  $x \cdot y = y \cdot x$

4. The distributive laws

$x$	$y$	$z$	$y+z$	$x \cdot (y+z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

# Postulates of Two-Valued Boolean Algebra

## 5. Complement

◆  $x + x' = 1 \rightarrow 0 + 0' = 0 + 1 = 1; 1 + 1' = 1 + 0 = 1$

◆  $x \cdot x' = 0 \rightarrow 0 \cdot 0' = 0 \cdot 1 = 0; 1 \cdot 1' = 1 \cdot 0 = 0$

## 6. Has two distinct elements 1 and 0, with $0 \neq 1$

### □ Note

◆ A set of two elements

◆  $(+)$  : OR operation;  $(\cdot)$  : AND operation

◆ A complement operator: NOT operation

◆ Binary logic is a two-valued Boolean algebra

## 2.4 Basic Theorems And Properties Of Boolean Algebra

# Duality

---

- The principle of *duality* is an important concept. This says that if an expression is valid in Boolean algebra, the dual of that expression is also valid.
- To form the dual of an expression, replace all (+) operators with (·) operators, all (·) operators with (+) operators, all ones with zeros, and all zeros with ones.
- Following the replacement rules...  
$$\mathbf{a(b + c) = ab + ac}$$
- Form the dual of the expression  
$$\mathbf{a + (bc) = (a + b)(a + c)}$$
- Take care not to alter the location of the parentheses if they are present.

# Basic Theorems

**Table 2.1**

*Postulates and Theorems of Boolean Algebra*

Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x'y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

# Boolean Theorems

- Huntington's postulates define some rules

Post. 1: closure

Post. 2: (a)  $x+0=x$ , (b)  $x \cdot 1=x$

Post. 3: (a)  $x+y=y+x$ , (b)  $x \cdot y=y \cdot x$

Post. 4: (a)  $x(y+z) = xy+xz$ ,  
(b)  $x+yz = (x+y)(x+z)$

Post. 5: (a)  $x+x'=1$ , (b)  $x \cdot x'=0$

- Need more rules to modify algebraic expressions

- ◆ Theorems that are derived from postulates

- What is a theorem?

- ◆ A formula or statement that is derived from postulates (or other proven theorems)

- Basic theorems of Boolean algebra

- ◆ Theorem 1 (a):  $x + x = x$  (b):  $x \cdot x = x$

- ◆ Looks straightforward, but needs to be proven !

# Proof of $x+x=x$

- We can only use Huntington postulates:

## Huntington postulates:

**Post. 2:** (a)  $x+0=x$ , (b)  $x \cdot 1=x$

**Post. 3:** (a)  $x+y=y+x$ , (b)  $x \cdot y=y \cdot x$

**Post. 4:** (a)  $x(y+z) = xy+xz$ ,  
(b)  $x+yz = (x+y)(x+z)$

**Post. 5:** (a)  $x+x'=1$ , (b)  $x \cdot x'=0$

- Show that  $x+x=x$ .

$$\begin{aligned}x+x &= (x+x) \cdot 1 && \text{by 2(b)} \\&= (x+x)(x+x') && \text{by 5(a)} \\&= x+xx' && \text{by 4(b)} \\&= x+0 && \text{by 5(b)} \\&= x && \text{by 2(a)}\end{aligned}$$

Q.E.D.

- We can now use Theorem 1(a) in future proofs

# Proof of $x \cdot x = x$

- ▣ Similar to previous proof

## Huntington postulates:

**Post. 2:** (a)  $x+0=x$ , (b)  $x \cdot 1=x$

**Post. 3:** (a)  $x+y=y+x$ , (b)  $x \cdot y=y \cdot x$

**Post. 4:** (a)  $x(y+z) = xy+xz$ ,  
(b)  $x+yz = (x+y)(x+z)$

**Post. 5:** (a)  $x+x'=1$ , (b)  $x \cdot x'=0$

**Th. 1:** (a)  $x+x=x$

- ▣ Show that  $x \cdot x = x$ .

$$x \cdot x = xx+0 \quad \text{by 2(a)}$$

$$= xx+xx \quad \text{by 5(b)}$$

$$= x(x+x') \quad \text{by 4(a)}$$

$$= x \cdot 1 \quad \text{by 5(a)}$$

$$= x \quad \text{by 2(b)}$$

Q.E.D.



# Proof of $x+1=1$

□ Theorem 2(a):  $x + 1 = 1$

$$\begin{aligned}x + 1 &= 1 \cdot (x + 1) && \text{by 2(b)} \\&= (x + x')(x + 1) && \text{5(a)} \\&= x + x'1 && \text{4(b)} \\&= x + x' && \text{2(b)} \\&= 1 && \text{5(a)}\end{aligned}$$

□ Theorem 2(b):  $x \cdot 0 = 0$  by duality

□ Theorem 3:  $(x')' = x$

- ◆ Postulate 5 defines the complement of  $x$ ,  $x + x' = 1$  and  $x x' = 0$
- ◆ The complement of  $x'$  is  $x$  is also  $(x')'$

Huntington postulates:

**Post. 2:** (a)  $x+0=x$ , (b)  $x \cdot 1=x$

**Post. 3:** (a)  $x+y=y+x$ , (b)  $x \cdot y=y \cdot x$

**Post. 4:** (a)  $x(y+z) = xy+xz$ ,  
(b)  $x+yz = (x+y)(x+z)$

**Post. 5:** (a)  $x+x'=1$ , (b)  $x \cdot x'=0$

**Th. 1:** (a)  $x+x=x$

# Absorption Property (Covering)

□ Theorem 6(a):  $x + xy = x$

$$\begin{aligned}
 &\blacklozenge x + xy = x \cdot 1 + xy && \text{by 2(b)} \\
 &= x(1 + y) && 4(a) \\
 &= x(y + 1) && 3(a) \\
 &= x \cdot 1 && \text{Th 2(a)} \\
 &= x && 2(b)
 \end{aligned}$$

Huntington postulates:

**Post. 2:** (a)  $x+0=x$ , (b)  $x \cdot 1=x$

**Post. 3:** (a)  $x+y=y+x$ , (b)  $x \cdot y=y \cdot x$

**Post. 4:** (a)  $x(y+z) = xy+xz$ ,  
(b)  $x+yz = (x+y)(x+z)$

**Post. 5:** (a)  $x+x'=1$ , (b)  $x \cdot x'=0$

**Th. 2:** (a)  $x+1=1$

□ Theorem 6(b):  $x(x + y) = x$  by duality

□ By means of truth table (another way to proof )

$x$	$y$	$xy$	$x+xy$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

# DeMorgan's Theorem

- Theorem 5(a):  $(x + y)' = x'y'$
- Theorem 5(b):  $(xy)' = x' + y'$
- By means of truth table

$x$	$y$	$x'$	$y'$	$x+y$	$(x+y)'$	$x'y'$	$xy$	$x'+y'$	$(xy)'$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

THE END

---

THE END

# Consensus Theorem

1.  $xy + x'z + yz = xy + x'z$
2.  $(x+y) \cdot (x'+z) \cdot (y+z) = (x+y) \cdot (x'+z)$  -- (dual)

## □ Proof:

◆  $xy + x'z + yz$

- »  $= xy + x'z + 1.yz$  2(a)
- »  $= xy + x'z + (x+x')yz$  5(a)
- »  $= xy + x'z + xyz + x'yz$  3(b) & 4(a)
- »  $= (xy + xyz) + (x'z + x'zy)$  Th4(a)
- »  $= x(y + yz) + x'(z + zy)$  4(a)
- »  $= xy + x'z$  Th6(a)
- » QED (2 true by duality).

# Operator Precedence

---

▣ The operator precedence for evaluating Boolean Expression is

- ◆ Parentheses
- ◆ NOT
- ◆ AND
- ◆ OR

▣ Examples

- ◆  $x y' + z$
- ◆  $(x y + z)'$

# 2.5 Boolean Functions

## □ A Boolean function

- ◆ Binary variables
- ◆ Binary operators OR and AND
- ◆ Unary operator NOT
- ◆ Parentheses

## □ Examples

- ◆  $F_1 = x y z'$
- ◆  $F_2 = x + y'z$
- ◆  $F_3 = x' y' z + x' y z + x y'$
- ◆  $F_4 = x y' + x' z$

# Boolean Functions

- The truth table of  $2^n$  entries (n=number of variables)

$x$	$y$	$z$	$F_1$	$F_2$	$F_3$	$F_4$
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

- Two Boolean expressions may specify the same function


- ◆  $F_3 = F_4$



# Boolean Functions

## Implementation with logic gates

◆  $F_4$  is more economical

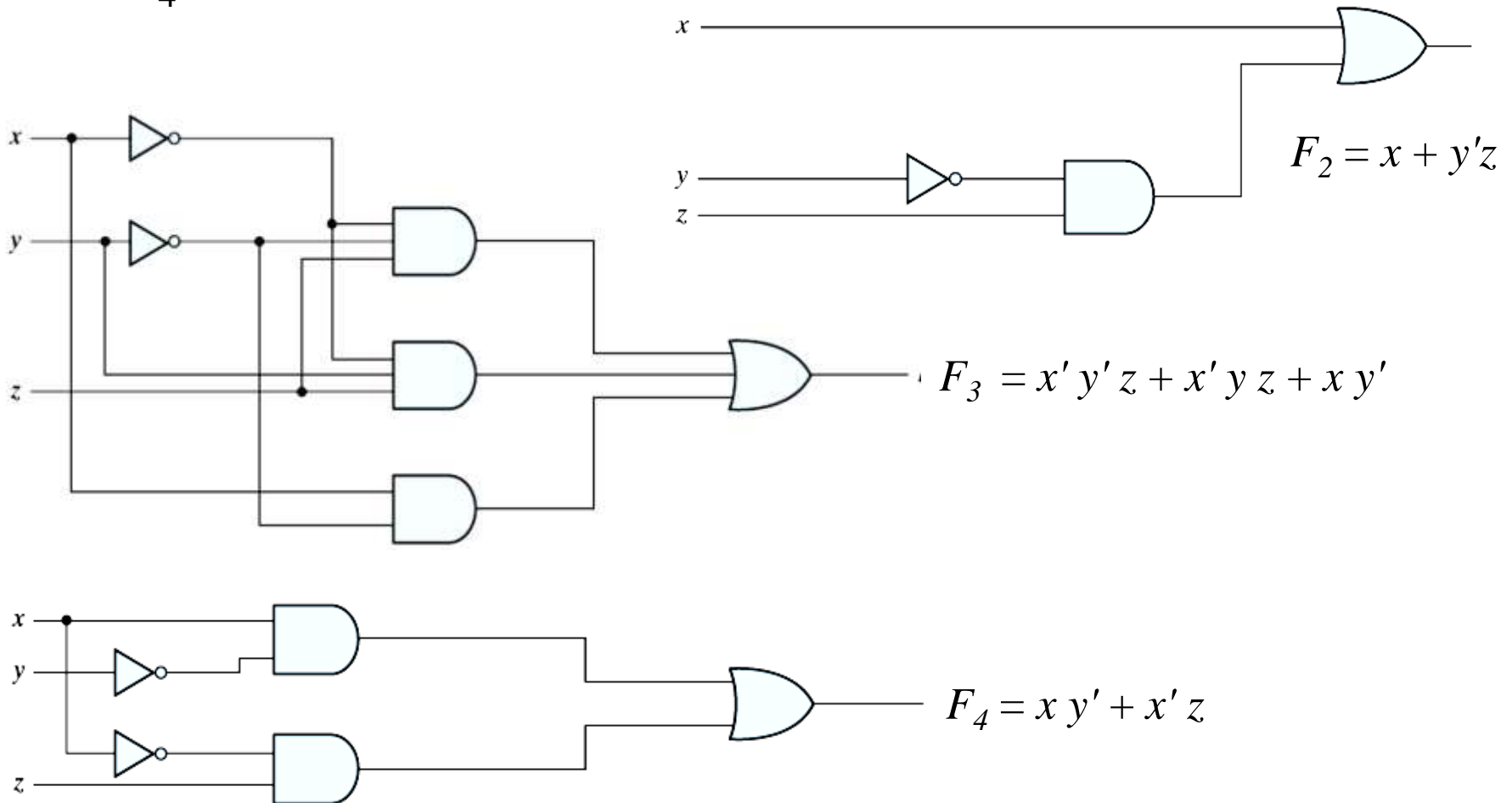

# Algebraic Manipulation

- When a Boolean expression is implemented with logic gates, each **term** requires a gate and each variable (**Literal**) within the term designates an input to the gate. (F3 has 3 terms and 8 literal)
- To minimize Boolean expressions, minimize the number of literals and the number of terms → a circuit with less equipment
  - ◆ It is a hard problem (no specific rules to follow)
- Example 2.1
  1.  $x(x'+y) = xx' + xy = 0 + xy = xy$
  2.  $x+x'y = (x+x')(x+y) = 1(x+y) = x+y$
  3.  $(x+y)(x+y') = x+xy+xy'+yy' = x(1+y+y') = x$
  4.  $xy + x'z + yz = xy + x'z + yz(x+x') = xy + x'z + yzx + yzx' = xy(1+z) + x'z(1+y) = xy + x'z$
  5.  $(x+y)(x'+z)(y+z) = (x+y)(x'+z)$ , by duality from function 4. (*consensus theorem* with duality)

# Complement of a Function

- An interchange of 0's for 1's and 1's for 0's in the value of  $F$

- ◆ By DeMorgan's theorem

- ◆  $(A+B+C)' = (A+X)'$       let  $B+C = X$   
 $= A'X'$       by theorem 5(a) (DeMorgan's)

- $= A'(B+C)'$       substitute  $B+C = X$   
 $= A'(B'C')$       by theorem 5(a)  
(DeMorgan's)

- $= A'B'C'$       by theorem 4(b) (associative)

- Generalization: a function is obtained by interchanging AND and OR operators and complementing each literal.

- ◆  $(A+B+C+D+ \dots +F)' = A'B'C'D' \dots F'$

- ◆  $(ABCD \dots F)' = A' + B' + C' + D' \dots + F'$

# Examples

## □ Example 2.2

$$◆ F_1' = (x'yz' + x'y'z)' = (x'yz')' (x'y'z)' = (x+y'+z) (x+y+z')$$

$$\begin{aligned} ◆ F_2' &= [x(y'z'+yz)]' = x' + (y'z'+yz)' = x' + (y'z')' (yz)' \\ &= x' + (y+z) (y'+z') \\ &= x' + yz' + y'z \end{aligned}$$

## □ Example 2.3: a simpler procedure

◆ **Take the dual of the function and complement each literal**

1.  $F_1 = x'yz' + x'y'z$ .

**The dual of  $F_1$  is  $(x'+y+z')(x'+y'+z)$ .**

**Complement each literal:  $(x+y'+z)(x+y+z') = F_1'$**

2.  $F_2 = x(y'z' + yz)$ .

**The dual of  $F_2$  is  $x+(y'+z')(y+z)$ .**

**Complement each literal:  $x'+(y+z)(y'+z') = F_2'$**

## 2.6 Canonical and Standard Forms

### Minterms and Maxterms

- ▣ A minterm (standard product): an AND term consists of all literals in their normal form or in their complement form.
  - ◆ For example, two binary variables  $x$  and  $y$ ,
    - »  $xy, xy', x'y, x'y'$
  - ◆ It is also called a standard product.
  - ◆  $n$  variables can be combined to form  $2^n$  minterms.
- ▣ A maxterm (standard sums): an OR term
  - ◆ It is also called a standard sum.
  - ◆  $2^n$  maxterms.

# Minterms and Maxterms

- Each *maxterm* is the complement of its corresponding *minterm*, and vice versa.

**Table 2.3**

*Minterms and Maxterms for Three Binary Variables*

<i>x</i>	<i>y</i>	<i>z</i>	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	$m_0$	$x + y + z$	$M_0$
0	0	1	$x'y'z$	$m_1$	$x + y + z'$	$M_1$
0	1	0	$x'yz'$	$m_2$	$x + y' + z$	$M_2$
0	1	1	$x'yz$	$m_3$	$x + y' + z'$	$M_3$
1	0	0	$xy'z'$	$m_4$	$x' + y + z$	$M_4$
1	0	1	$xy'z$	$m_5$	$x' + y + z'$	$M_5$
1	1	0	$xyz'$	$m_6$	$x' + y' + z$	$M_6$
1	1	1	$xyz$	$m_7$	$x' + y' + z'$	$M_7$

# Minterms and Maxterms

■ An Boolean function can be expressed by

- ◆ A truth table
- ◆ Sum of minterms for each combination of variables that produces a (1) in the function.
- ◆  $f_1 = x'y'z + xy'z' + xyz = m_1 + m_4 + m_7$  (Minterms)
- ◆  $f_2 = x'yz + xy'z + xyz' + xyz = m_3 + m_5 + m_6 + m_7$  (Minterms)

**Table 2.4**

*Functions of Three Variables*

<b>x</b>	<b>y</b>	<b>z</b>	<b>Function <math>f_1</math></b>	<b>Function <math>f_2</math></b>
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Minterms and Maxterms

## □ The complement of a Boolean function

◆ The minterms that produce a 0

◆  $f_1' = m_0 + m_2 + m_3 + m_5 + m_6 = x'y'z' + x'yz' + x'yz + xy'z + xyz'$

◆  $f_1 = (f_1')'$

◆  $= (x+y+z)(x+y'+z)(x+y'+z')(x'+y+z')(x'+y'+z) = M_0 M_2 M_3 M_5 M_6$

◆  $f_2 = (x+y+z)(x+y+z')(x+y'+z)(x'+y+z) = M_0 M_1 M_2 M_4$

◆ Any Boolean function can be expressed as terms).

◆ A product of maxterms (“product” meaning the ANDing of terms).

◆ A sum of minterms (“sum” meaning the ORing of Both boolean functions are said to be in Canonical form.



# Sum of Minterms

- ▣ Sum of minterms: there are  $2^n$  minterms and  $2^{2n}$  combinations of functions with  $n$  Boolean variables.
- ▣ Example 2.4: express  $F = A + B'C$  as a sum of minterms.
  - ◆  $F = A + B'C = A(B + B') + B'C = AB + AB' + B'C = AB(C + C') + AB'(C + C') + (A + A')B'C = ABC + ABC' + AB'C + AB'C' + A'B'C$
  - ◆  $F = A'B'C + AB'C' + AB'C + ABC' + ABC = m_1 + m_4 + m_5 + m_6 + m_7$
  - ◆  $F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$
  - ◆ or, built the truth table first

**Table 2.5**

Truth Table for  $F = A + B'C$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

# Product of Maxterms

▣ Product of maxterms: using distributive law to expand.

$$\blacklozenge x + yz = (x + y)(x + z) = (x+y+zz')(x+z+yy') = (x+y+z)(x+y+z')(x+y'+z)$$

▣ Example 2.5: express  $F = xy + x'z$  as a product of maxterms.

$$\blacklozenge F = xy + x'z = (xy + x')(xy + z) = (x+x')(y+x')(x+z)(y+z) = (x'+y)(x+z)(y+z)$$

$$\blacklozenge x' + y = x' + y + zz' = (x' + y + z)(x' + y + z')$$

$$\blacklozenge F = (x+y+z)(x+y'+z)(x'+y+z)(x'+y+z') = M_0 M_2 M_4 M_5$$

$$\blacklozenge F(x, y, z) = \Pi(0, 2, 4, 5)$$

# Conversion between Canonical Forms

- ▣ The complement of a function expressed as the sum of minterms equals the sum of minterms missing from the original function.

- ◆  $F(A, B, C) = \Sigma(1, 4, 5, 6, 7)$

- ◆ Thus,  $F'(A, B, C) = \Sigma(0, 2, 3)$

- ◆ By DeMorgan's theorem

$$F(A, B, C) = \Pi(0, 2, 3)$$

$$F'(A, B, C) = \Pi(1, 4, 5, 6, 7)$$

- ◆  $m_j' = M_j$

- ▣ To convert from one canonical form to another: **interchange** the symbols  $\Sigma$  and  $\Pi$  and list those numbers **missing** from the original form

- »  $\Sigma$  of 1's

- »  $\Pi$  of 0's

## □ Example

- ◆  $F = xy + x'z$
- ◆  $F(x, y, z) = \Sigma(1, 3, 6, 7)$
- ◆  $F(x, y, z) = \Pi(0, 2, 4, 6)$

**Table 2.6**

*Truth Table for  $F = xy + x'z$*


<b>x</b>	<b>y</b>	<b>z</b>	<b>F</b>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

# Standard Forms


- In canonical forms each minterm or maxterm must contain **all the variables** either complemented or uncomplemented, thus these forms are very seldom the ones with the least number of literals.
- Standard forms: the terms that form the function may obtain **one, two, or any number** of literals, .There are two types of standard forms:
  - ◆ Sum of products:  $F_1 = y' + xy + x'yz'$
  - ◆ Product of sums:  $F_2 = x(y' + z)(x' + y + z')$
- A Boolean function may be expressed in a nonstandard form
  - ◆  $F_3 = AB + C(D + E)$
- But it can be changed to a standard form by using The distributive law
  - ◆  $F_3 = AB + C(D + E) = AB + CD + CE$

# Implementation

## Two-level implementation

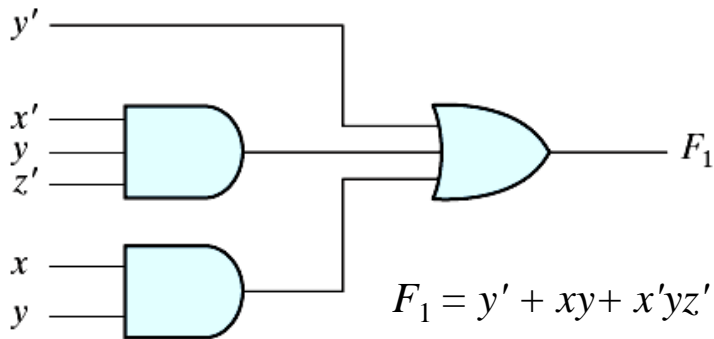


(a) Sum of Products

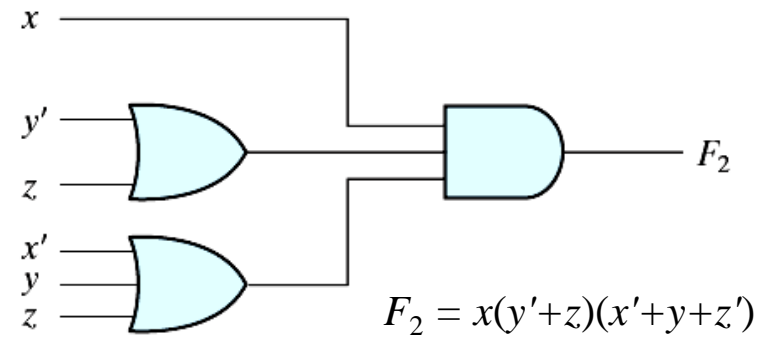


(b) Product of Sums

## Multi-level implementation

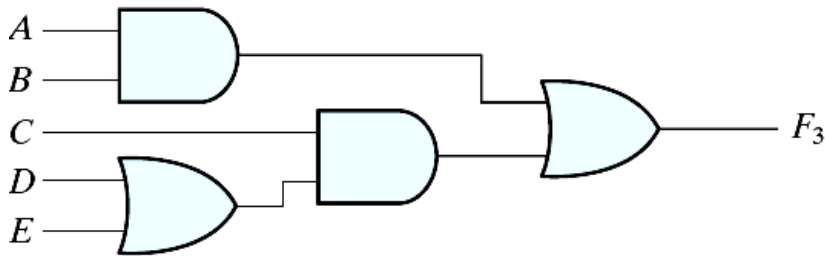

(a)  $AB + C(D + E)$

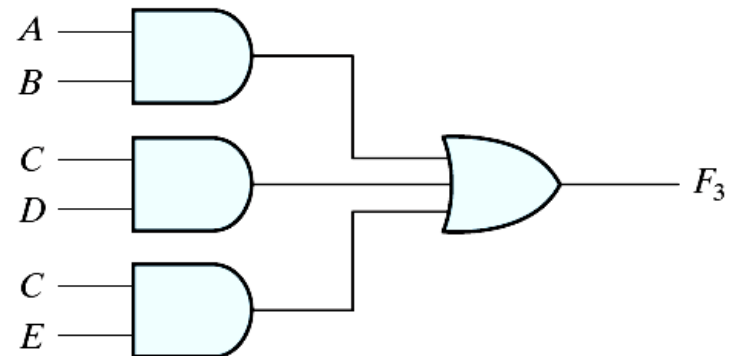

(b)  $AB + CD + CE$

## 2.7 Other Logic Operations

- $2^n$  rows in the truth table of  $n$  binary variables.
- $2^{2^n}$  functions for  $n$  binary variables.
- 16 functions of two binary variables.

**Table 2.7**

*Truth Tables for the 16 Functions of Two Binary Variables*

$x$	$y$	$F_0$	$F_1$	$F_2$	$F_3$	$F_4$	$F_5$	$F_6$	$F_7$	$F_8$	$F_9$	$F_{10}$	$F_{11}$	$F_{12}$	$F_{13}$	$F_{14}$	$F_{15}$
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

- All the new symbols except for the exclusive-OR symbol are not in common use by digital designers.

# Boolean Expressions

**Table 2.8**

*Boolean Expressions for the 16 Functions of Two Variables*

Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	$x$ and $y$
$F_2 = xy'$	$x/y$	Inhibition	$x$ , but not $y$
$F_3 = x$		Transfer	$x$
$F_4 = x'y$	$y/x$	Inhibition	$y$ , but not $x$
$F_5 = y$		Transfer	$y$
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	$x$ or $y$ , but not both
$F_7 = x + y$	$x + y$	OR	$x$ or $y$
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	$x$ equals $y$
$F_{10} = y'$	$y'$	Complement	Not $y$
$F_{11} = x + y'$	$x \subset y$	Implication	If $y$ , then $x$
$F_{12} = x'$	$x'$	Complement	Not $x$
$F_{13} = x' + y$	$x \supset y$	Implication	If $x$ , then $y$
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1



## 2.8 Digital Logic Gates

---

- ▣ Boolean expression: AND, OR and NOT operations
- ▣ Constructing gates of other logic operations
  - ◆ The feasibility and economy;
  - ◆ The possibility of extending gate's inputs;
  - ◆ The basic properties of the binary operations (commutative and associative);
  - ◆ The ability of the gate to implement Boolean functions.

# Standard Gates

## ■ Consider the 16 functions in Table 2.8


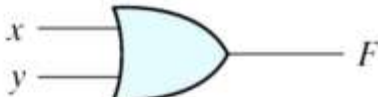
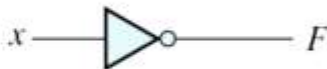
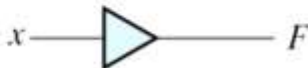
- ◆ **Two** functions produce a constant : ( $F_0$  and  $F_{15}$ ).
- ◆ **Four** functions with unary operations: complement and transfer: ( $F_3$ ,  $F_5$ ,  $F_{10}$  and  $F_{12}$ ).
- ◆ The other **ten** functions with binary operators

## ■ Eight function are used as standard gates :

complement ( $F_{12}$ ), transfer ( $F_3$ ), AND ( $F_1$ ), OR ( $F_7$ ), NAND ( $F_{14}$ ), NOR ( $F_8$ ), XOR ( $F_6$ ), and equivalence (XNOR) ( $F_9$ ).

- ◆ Complement: inverter.
- ◆ Transfer: buffer (increasing drive strength).
- ◆ Equivalence: XNOR.

# Summary of Logic Gates

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = xy$	<table><tr><th><math>x</math></th><th><math>y</math></th><th><math>F</math></th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	$x$	$y$	$F$	0	0	0	0	1	0	1	0	0	1	1	1
$x$	$y$	$F$																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th><math>x</math></th><th><math>y</math></th><th><math>F</math></th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	$x$	$y$	$F$	0	0	0	0	1	1	1	0	1	1	1	1
$x$	$y$	$F$																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th><math>x</math></th><th><math>F</math></th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	$x$	$F$	0	1	1	0									
$x$	$F$																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th><math>x</math></th><th><math>F</math></th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	$x$	$F$	0	0	1	1									
$x$	$F$																	
0	0																	
1	1																	

**Figure 2.5 Digital logic gates**

# Summary of Logic Gates


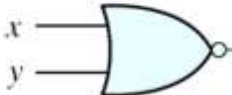
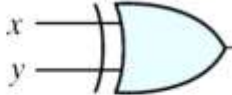
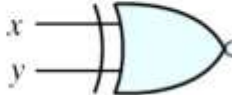
NAND	 $F = (xy)'$	<table> <tr> <th><math>x</math></th><th><math>y</math></th><th><math>F</math></th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	$x$	$y$	$F$	0	0	1	0	1	1	1	0	1	1	1	0
$x$	$y$	$F$															
0	0	1															
0	1	1															
1	0	1															
1	1	0															
NOR	 $F = (x + y)'$	<table> <tr> <th><math>x</math></th><th><math>y</math></th><th><math>F</math></th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	$x$	$y$	$F$	0	0	1	0	1	0	1	0	0	1	1	0
$x$	$y$	$F$															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
Exclusive-OR (XOR)	 $F = xy' + x'y$ $= x \oplus y$	<table> <tr> <th><math>x</math></th><th><math>y</math></th><th><math>F</math></th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	$x$	$y$	$F$	0	0	0	0	1	1	1	0	1	1	1	0
$x$	$y$	$F$															
0	0	0															
0	1	1															
1	0	1															
1	1	0															
Exclusive-NOR or equivalence	 $F = xy + x'y'$ $= (x \oplus y)'$	<table> <tr> <th><math>x</math></th><th><math>y</math></th><th><math>F</math></th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	$x$	$y$	$F$	0	0	1	0	1	0	1	0	0	1	1	1
$x$	$y$	$F$															
0	0	1															
0	1	0															
1	0	0															
1	1	1															

Figure 2.5 Digital logic gates


# Multiple Inputs

## □ Extension to multiple inputs


- ◆ A gate can be extended to multiple inputs.
  - » If its binary operation is commutative and associative.
- ◆ AND and OR are commutative and associative.
  - » OR
    - $x+y = y+x$
    - $(x+y)+z = x+(y+z) = x+y+z$
  - » AND
    - $xy = yx$
    - $(x y)z = x(y z) = x y z$
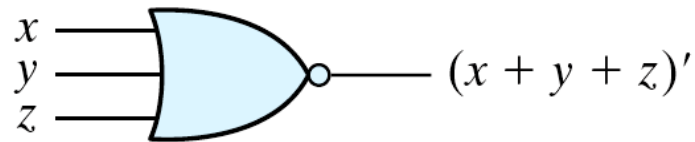
# Multiple Inputs


- Multiple NOR = a complement of OR gate, Multiple NAND = a complement of AND.
- The cascaded NAND operations = sum of products.
- The cascaded NOR operations = product of sums.



(a) 3-input NOR gate

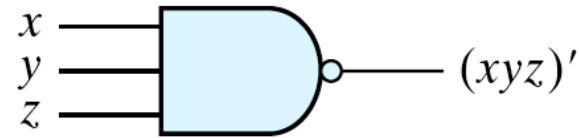

(b) 3-input NAND gate

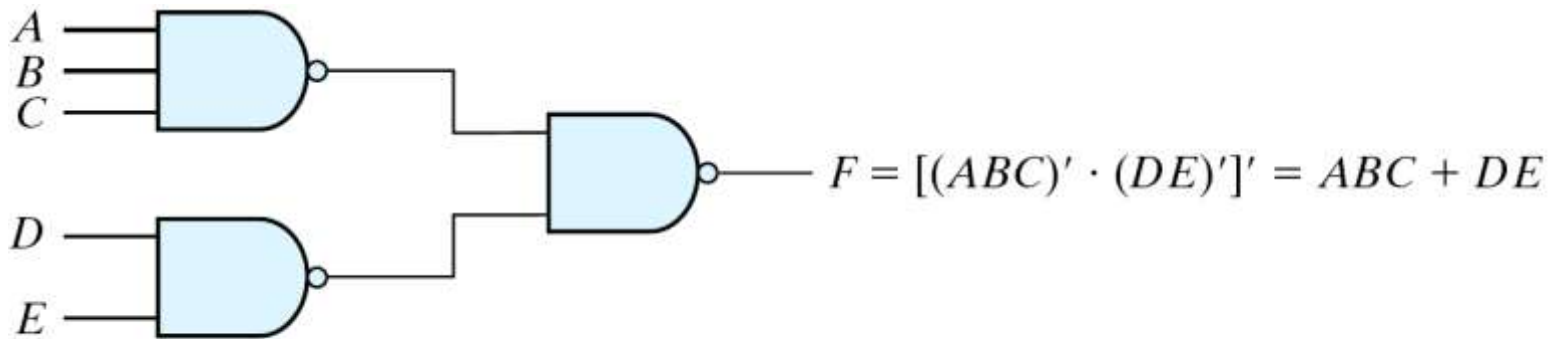


(c) Cascaded NAND gates


**Figure 2.7 Multiple-input and cascaded NOR and NAND gates**
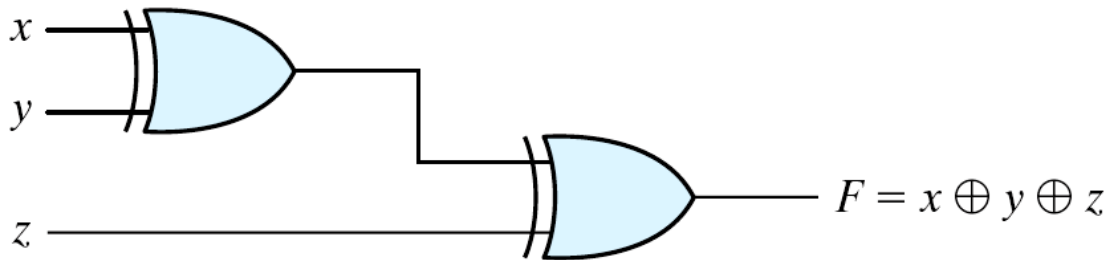
# Multiple Inputs

- The XOR and XNOR gates are commutative and associative.
- Multiple-input XOR gates are uncommon?
- XOR is an odd function: it is equal to 1 if the inputs variables have an odd number of 1's.



(a) Using 2-input gates

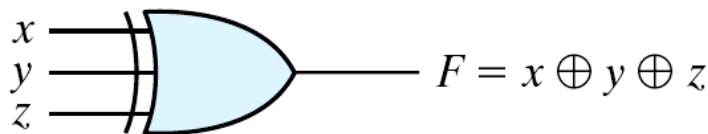

(b) 3-input gate

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table

**Figure 2.8 3-input XOR gate**


# Positive and Negative Logic

## Positive and Negative Logic

- ◆ Two signal values  $\Leftrightarrow$  two logic values
- ◆ Positive logic:  $H=1$ ;  $L=0$
- ◆ Negative logic:  $H=0$ ;  $L=1$
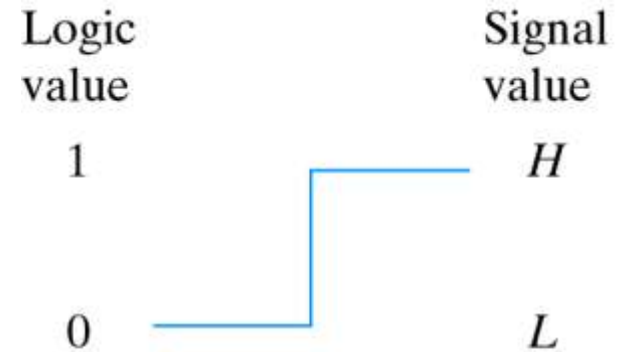
## Consider a TTL gates

- ◆ A positive logic AND gate
- ◆ A negative logic OR gate



(a) Positive logic



(b) Negative logic

**Figure 2.9 Signal assignment and logic polarity**



# Positive and Negative Logic

$x$	$y$	$z$
$L$	$L$	$L$
$L$	$H$	$L$
$H$	$L$	$L$
$H$	$H$	$H$


(a) Truth table with  $H$  and  $L$

$x$	$y$	$z$
0	0	0
0	1	0
1	0	0
1	1	1


(c) Truth table for positive logic

$x$	$y$	$z$
1	1	1
1	0	1
0	1	1
0	0	0


(e) Truth table for negative logic

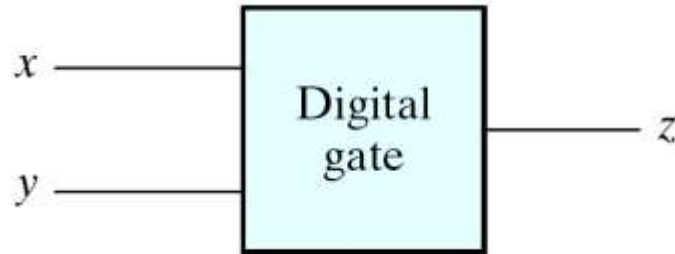

(b) Gate block diagram

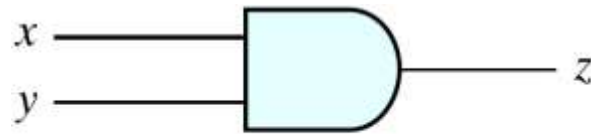

(d) Positive logic AND gate

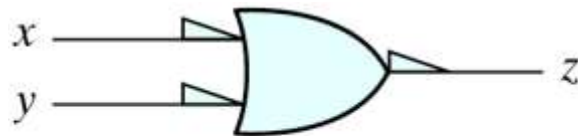

(f) Negative logic OR gate

**Figure 2.10 Demonstration of positive and negative logic**

## 2.9 Integrated Circuits

### Level of Integration

- An IC (a chip)

- Examples:

- ◆ Small-scale Integration (SSI):  $< 10$  gates
- ◆ Medium-scale Integration (MSI):  $10 \sim 100$  gates
- ◆ Large-scale Integration (LSI):  $100 \sim \text{xk}$  gates
- ◆ Very Large-scale Integration (VLSI):  $> \text{xk}$  gates

- VLSI

- ◆ Small size (compact size)
- ◆ Low cost
- ◆ Low power consumption
- ◆ High reliability
- ◆ High speed

# Digital Logic Families

---

- ▣ Digital logic families: circuit technology
  - ◆ TTL: transistor-transistor logic (dying?)
  - ◆ ECL: emitter-coupled logic (high speed, high power consumption)
  - ◆ MOS: metal-oxide semiconductor (NMOS, high density)
  - ◆ CMOS: complementary MOS (low power)
  - ◆ BiCMOS: high speed, high density

# Digital Logic Families

---

## □ The characteristics of digital logic families

- ◆ Fan-out: the number of standard loads that the output of a typical gate can drive.
- ◆ Power dissipation.
- ◆ Propagation delay: the average transition delay time for the signal to propagate from input to output.
- ◆ Noise margin: the minimum of external noise voltage that caused an undesirable change in the circuit output.

# CAD

---

## ▣ CAD – Computer-Aided Design

- ◆ Software programs that support computer-based representation of circuits of millions of gates.
- ◆ Automate the design process
- ◆ Two design entry:
  - » Schematic capture
  - » HDL – Hardware Description Language
    - Verilog, VHDL
- ◆ Simulation
- ◆ Physical realization

# Home Work (4)

---

Digital Design (**4<sup>th</sup>**)- Morris Mano-Page 66-  
Problems:

2.3 d,f

2.4 d,e

2.6 Only for (2.3 d,f)

2.7 Only for (2.4 d,f)

2.9

2.20

2.22

# Home Work (5)

---

Digital Design (**4<sup>th</sup>**)- Morris Mano-Page 66-  
Problems:

2.13

2.14

2.15

2.27

2.28